

تم تحميل هذا الملف من موقع المناهج الإماراتية



*للحصول على أوراق عمل لجميع الصفوف وجميع المواد اضغط هنا

<https://almanahj.com/ae>

* للحصول على أوراق عمل لجميع مواد الصف الثاني عشر المتقدم اضغط هنا

<https://almanahj.com/ae/15>

* للحصول على جميع أوراق الصف الثاني عشر المتقدم في مادة فيزياء وجميع الفصول, اضغط هنا

<https://almanahj.com/ae/15physics>

* للحصول على أوراق عمل لجميع مواد الصف الثاني عشر المتقدم في مادة فيزياء الخاصة بـ الفصل الثالث اضغط هنا

<https://almanahj.com/ae/15physics3>

* لتحميل كتب جميع المواد في جميع الفصول للـ الصف الثاني عشر المتقدم اضغط هنا

<https://almanahj.com/ae/grade15>

* لتحميل جميع ملفات المدرس رامي عبد الفتاح اضغط هنا

للتحدث إلى بوت المناهج على تلغرام: اضغط هنا

https://t.me/almanahj_bot


ALTERNATIVE CURRENT PROBLEMS & ANSWERS

إعداد الأستاذ/ رامي عبد الفتاح

0507292077

قناة التليجرام

@einstien_gulf_in_physics

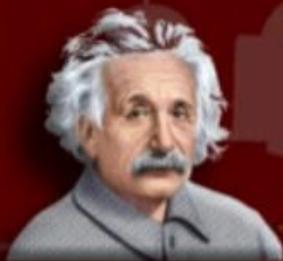

سلسلة أينشتاين الخليج

A 100 Ω resistor is connected to a 220 V, 50 Hz ac supply.

- (a) What is the rms value of current in the circuit?
(b) What is the net power consumed over a full cycle?

Answer

Resistance of the resistor, $R = 100 \Omega$, Supply voltage, $V = 220 \text{ V}$, Frequency, $\nu = 50 \text{ Hz}$

- (a) The rms value of current in the circuit is given as

$$I = \frac{V}{R} = \frac{220}{100} = 2.20 \text{ A}$$

- (b) The net power consumed over a full cycle is given as: $P = VI = 220 \times 2.2 = 484 \text{ W}$

- (a) The peak voltage of an ac supply is 300 V. What is the rms voltage?

- (b) The rms value of current in an ac circuit is 10 A. What is the peak current?

Answer

- (a) Peak voltage of the ac supply, $V_0 = 300 \text{ V}$, rms voltage is given as:

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{300}{\sqrt{2}} = 212.1 \text{ V}$$

- (c) The rms value of current is given as: $I = 10 \text{ A}$

Now, peak current is given as: $I_0 = \sqrt{2}I = \sqrt{2} \times 10 = 14.1 \text{ A}$

A 44 mH inductor is connected to 220 V, 50 Hz ac supply. Determine the rms value of the current in the circuit.

Answer

Inductance of inductor, $L = 44 \text{ mH} = 44 \times 10^{-3} \text{ H}$

Supply voltage, $V = 220 \text{ V}$, Frequency, $\nu = 50 \text{ Hz}$, Angular frequency, $\omega = 2\pi\nu$

Inductive reactance, $X_L = \omega L = 2\pi\nu L = 2\pi \times 50 \times 44 \times 10^{-3} \Omega$

rms value of current is given as:

$$I = \frac{V}{X_L} = \frac{220}{2\pi \times 50 \times 44 \times 10^{-3}} = 15.92 \text{ A}$$

Hence, the rms value of current in the circuit is 15.92 A.

A 60 μF capacitor is connected to 110 V, 60 Hz ac supply. Determine the rms value of the current in the circuit.

Answer

Capacitance of capacitor, $C = 60 \mu\text{F} = 60 \times 10^{-6} \text{ F}$

Supply voltage, $V = 110 \text{ V}$

Frequency, $\nu = 60 \text{ Hz}$

Angular frequency, $\omega = 2\pi\nu$


Capacitive reactance,

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi\nu C} = \frac{1}{2\pi \times 60 \times 60 \times 10^{-6}} \Omega$$

rms value of current is given as:

$$I = \frac{V}{X_C} = \frac{110}{2\pi \times 60 \times 60 \times 10^{-6}} = 2.49 \text{ A}$$

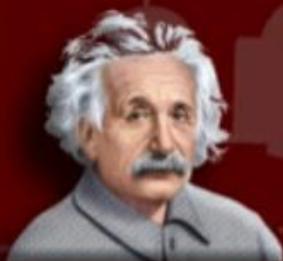Hence, the rms value of current is 2.49 A.



In Exercises 7.3 and 7.4, what is the net power absorbed by each circuit over a complete cycle. Explain your answer.

Answer

In the inductive circuit,
rms value of current, $I = 15.92 \text{ A}$
rms value of voltage, $V = 220 \text{ V}$

Hence, the net power absorbed can be obtained by the relation,

$$P = VI \cos \Phi$$

Where, Φ = Phase difference between V and I .

For a pure inductive circuit, the phase difference between alternating voltage and current is 90° i.e., $\Phi = 90^\circ$.

Hence, $P = 0$ i.e., the net power is zero.

In the capacitive circuit, rms value of current, $I = 2.49 \text{ A}$, rms value of voltage, $V = 110 \text{ V}$

Hence, the net power absorbed can be obtained as:

$$P = VI \cos \Phi$$

For a pure capacitive circuit, the phase difference between alternating voltage and current is 90° i.e., $\Phi = 90^\circ$.

Hence, $P = 0$ i.e., the net power is zero.

Obtain the resonant frequency ω_r of a series LCR circuit with $L = 2.0 \text{ H}$, $C = 32 \mu\text{F}$ and $R = 10 \Omega$. What is the Q-value of this circuit?

Answer

Inductance, $L = 2.0 \text{ H}$
Capacitance, $C = 32 \mu\text{F} = 32 \times 10^{-6} \text{ F}$
Resistance, $R = 10 \Omega$

Resonant frequency is given by the relation,

$$\omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2.0 \times 32 \times 10^{-6}}} = \frac{1}{8 \times 10^{-3}} = 125 \text{ rad/s.}$$


Now, Q-value of the circuit is given as:

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{2}{32 \times 10^{-6}}} = \frac{1}{10 \times 4 \times 1}$$

Hence, the Q-Value of this circuit is 25.

قناة التليجرام

@einstien_gulf_in_physics

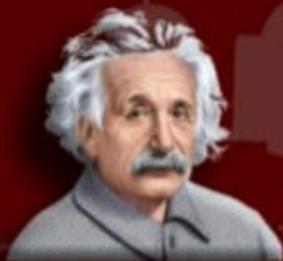

سلسلة أينشتاين الخليج