

تم تحميل هذا الملف من موقع المناهج الإماراتية



\*للحصول على أوراق عمل لجميع الصفوف وجميع المواد اضغط هنا

<https://almanahj.com/ae>

\* للحصول على أوراق عمل لجميع مواد الصف الثاني عشر المتقدم اضغط هنا

<https://almanahj.com/ae/15>

\* للحصول على جميع أوراق الصف الثاني عشر المتقدم في مادة فيزياء وجميع الفصول, اضغط هنا

<https://almanahj.com/ae/15>

\* للحصول على أوراق عمل لجميع مواد الصف الثاني عشر المتقدم في مادة فيزياء الخاصة بـ اضغط هنا

<https://almanahj.com/ae/15>

\* لتحميل كتب جميع المواد في جميع الفصول للصف الثاني عشر المتقدم اضغط هنا

<https://almanahj.com/ae/grade15>


للتحدث إلى بوت المناهج على تلغرام: اضغط هنا

[https://t.me/almanahj\\_bot](https://t.me/almanahj_bot)


# Alternating-Current Circuits

## CH (10)


Al Dahma' Secondary School  
Alain

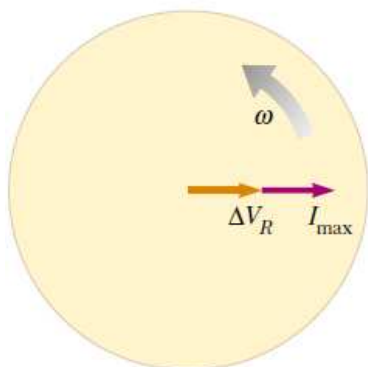

(a) Resistor

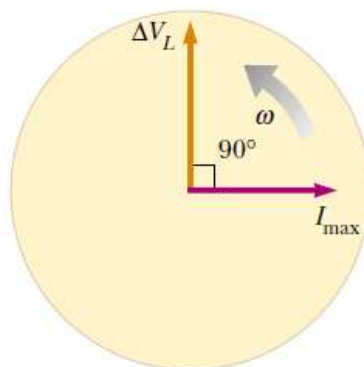

(b) Inductor

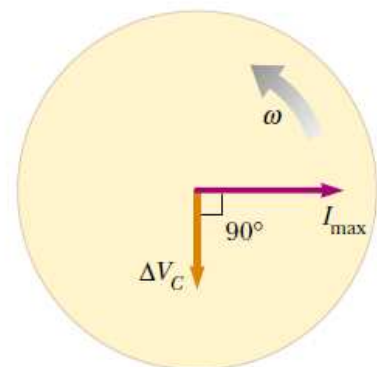

(c) Capacitor

Circuit Elements	Impedance $Z$	Phase Angle $\phi$
	$R$	$0^\circ$
	$X_C$	$-90^\circ$
	$X_L$	$+90^\circ$
	$\sqrt{R^2 + X_C^2}$	Negative, between $-90^\circ$ and $0^\circ$
	$\sqrt{R^2 + X_L^2}$	Positive, between $0^\circ$ and $90^\circ$
	$\sqrt{R^2 + (X_L - X_C)^2}$	Negative if $X_C > X_L$ Positive if $X_C < X_L$

1. The power is transmitted from a powerhouse on high voltage AC because:
  - A) Electric current travels faster at higher volts
  - B) It is more economical due to less power wastage
  - C) It is difficult to generate power at low voltage
  - D) Chances of stealing transmission lines are minimized
  
2. The potential difference  $V$  and the current  $i$  flowing through an instrument in an AC circuit of frequency  $f$  are given by  $V = 5.0 \cos \omega t$  volts and  $i = 2.0 \sin \omega t$  amperes (where  $\omega = 2\pi f$ ). The power dissipated in the instrument is:
  - A) Zero
  - B) 10 W
  - C) 5 W
  - D) 2.5 W
  
3. In an AC circuit,  $V$  and  $i$  are given by  $V = 100 \sin(100t)$  volts,  $i = 100 \sin(100t + \frac{\pi}{3})$  mA. The power dissipated in circuit is:
  - A) 104 watt
  - B) 10 watt
  - C) 2.5 watt
  - D) 5 watt
  
4. The resistance of a coil for DC is in ohms. In AC, the resistance:
  - A) Will remain same
  - B) Will increase
  - C) Will decrease
  - D) Will be zero
  
5. If instantaneous current is given by  $i = 4 \cos(\omega t + \varphi)$  A, then the r.m.s. value of current is:
  - A) 4 A
  - B)  $2\sqrt{2}$  A
  - C)  $4\sqrt{2}$  A
  - D) Zero A
  
6. In an AC circuit  $i = 100 \sin 200 \pi t$ . The time required for the current to achieve its peak value will be:
  - A)  $\frac{1}{100}$  s
  - B)  $\frac{1}{200}$  s
  - C)  $\frac{1}{300}$  s
  - D)  $\frac{1}{400}$  s



7. A generator produces a voltage that is given by  $V = 240\sin 120t$ , where  $t$  is in seconds. The frequency and r.m.s. voltage are:
- A) 60 Hz and 240 V  
 B) 19 Hz and 120 V  
 C) 19 Hz and 170 V  
 D) 754 Hz and 70 V
8. If  $V_0$  represents the peak value of the voltage in an AC circuit, the r.m.s. value of the voltage will be:
- A)  $\frac{V_0}{\pi}$   
 B)  $\frac{V_0}{2}$   
 C)  $\frac{V_0}{\sqrt{\pi}}$   
 D)  $\frac{V_0}{\sqrt{2}}$
9. The peak value of 220 V of AC mains is:
- A) 155.6 V  
 B) 220.0 V  
 C) 311.0 V  
 D) 440 V
10. A sinusoidal AC current flows through a resistor of resistance  $R$ . If the peak current is  $i_p$ , then the power dissipated is:
- A)  $i_p^2 R \cos \theta$   
 B)  $\frac{1}{2} i_p^2 R$   
 C)  $\frac{4}{\pi} i_p^2 R$   
 D)  $\frac{1}{\pi} i_p^2 R$
11. A 40 W electric heater is connected to a 200 V, 50 Hz mains supply. The peak value of electric current flowing in the circuit is approximately:
- A) 2.5 A  
 B) 5.0 A  
 C) 7 A  
 D) 10 A
12. The root mean square value of the alternating current is equal to:
- A) Twice the peak value  
 B) Half the peak value  
 C)  $\frac{1}{\sqrt{2}}$  times the peak value  
 D) Equal to the peak value
13. The peak value of an alternating e.m.f.  $V$  is given by  $V = V_0 \cos \omega t$  is 10 volts and its frequency is 50 Hz. At time  $t = 1600\text{s}$ , the instantaneous e.m.f. is:
- A) 10 V  
 B)  $5\sqrt{3}$  V  
 C) 5 V  
 D) 1 V





14. An AC generator produced an output voltage  $V = 170\sin 377t$  V, where  $t$  is in seconds. The frequency of AC voltage is:
- A) 50 Hz
  - B) 110 Hz
  - C) 60 Hz
  - D) 230 Hz
15. In general, in an alternating current circuit:
- A) The average value of current is zero
  - B) The average value of square of the current is zero
  - C) Average power dissipation is zero
  - D) The phase difference between voltage and current is zero
16. The r. m. s. voltage of domestic electricity supply is 220 V . Electrical appliances should be designed to withstand an instantaneous voltage of:
- A) 220 V
  - B) 310 V
  - C) 330 V
  - D) 440 V
17. The process by which AC is converted into DC is known as:
- A) Purification
  - B) Amplification
  - C) Rectification
  - D) Current amplification
18. For an AC circuit  $V = 15\sin\omega t$  and  $i = 20\cos\omega t$  the average power consumed in this circuit is:
- A) 300 Watt
  - B) 150 Watt
  - C) 75 Watt
  - D) zero
19. A bulb is connected first with DC and then AC of same voltage then it will shine brightly with:
- A) AC
  - B) DC
  - C) Brightness will be in ratio 1/1.4
  - D) Equally with both
20. The frequency of an alternating voltage is 50 cycles/sec and its amplitude is 120V. Then the r. m. s. value of voltage is:
- A) 101.3V
  - B) 84.8V
  - C) 70.7V
  - D) 56.5V



21. A resistance of  $20 \Omega$  is connected to a source of an alternating potential  $V = 220\sin(100\pi t)$ . The time taken by the current to change from its peak value to *r. m. s* value is:
- A)  $0.2 \text{ s}$   
 B)  $0.25 \text{ s}$   
 C)  $25 \times 10^{-3} \text{ s}$   
 D)  $2.5 \times 10^{-3} \text{ s}$
22. Voltage and current in an AC circuit are given by  $V = 5\sin(100\pi t - \pi/6)$  and  $i = 4\sin(100\pi t + \frac{\pi}{6})$
- A) Voltage leads the current by  $30^\circ$   
 B) Current leads the voltage by  $30^\circ$   
 C) Current leads the voltage by  $60^\circ$   
 D) Voltage leads the current by  $60^\circ$
23. The ratio of peak value and *r. m. s* value of an alternating current is:
- A) 1  
 B)  $\frac{1}{2}$   
 C)  $\sqrt{2}$   
 D)  $\frac{1}{\sqrt{2}}$
24. If an alternating voltage is represented as  $V = 141\sin(628t)$ , then the rms value of the voltage and the frequency are respective:
- A)  $141V, 628Hz$   
 B)  $100V, 50Hz$   
 C)  $100V, 100Hz$   
 D)  $141V, 100Hz$
25. Current in the circuit is **wattles**, if:
- A) Inductance in the circuit is zero  
 B) Resistance in the circuit is zero  
 C) Current is alternating  
 D) Resistance and inductance both are zero
26. A circuit containing capacitance only. An alternating *e. m. f.* is applied to purely capacitive circuit. **The phase relation** between *e. m. f.* and *current flowing* in the circuit is:
- A) *e. m. f.* is leads the current by  $(\frac{\pi}{2})$   
 B) Current is leads the *e. m. f.* by  $(\frac{\pi}{2})$   
 C) Current lags behind *e. m. f.* by  $(\pi)$   
 D) Current is leads the *e. m. f.* by  $(\pi)$
27. An AC source is connected to a resistive circuit. Which of the following is true?
- A) Current leads the voltage and both are in same phase  
 B) Current lags behind the voltage and both are in same phase  
 C) Current and voltage are in same phase  
 D) Any of the above may be true depending upon the value of resistance



28. The phase angle between *e. m. f.* and *current(i)* in *LCR* series ac circuit is:

- A) 0 to  $\left(\frac{\pi}{2}\right)$
- B)  $\left(\frac{\pi}{4}\right)$
- C)  $\left(\frac{\pi}{2}\right)$
- D)  $\pi$

29. The average power dissipated in a pure inductor of inductance *L* when an *AC* current is passing through it, is:

- A)  $\frac{1}{2} Li^2$
- B)  $\frac{1}{4} Li^2$
- C)  $2Li^2$
- D) Zero

30. An alternating current of frequency '*f*' is flowing in a circuit containing a resistance *R* and a choke *L* in series. The **impedance**(*Z*) of this circuit is:

- A)  $R + 2\pi fL$
- B)  $\sqrt{R^2 + 4\pi^2 f^2 L^2}$
- C)  $\sqrt{R^2 + L^2}$
- D)  $\sqrt{R^2 + 2\pi fL}$

31. A resonant *AC* circuit contains a capacitor of capacitance  $10^{-6}F$  and an inductor of  $10^{-4}H$ . The *frequency* of electrical oscillations will be:

- A)  $10^5 Hz$
- B)  $10 Hz$
- C)  $\frac{10^5}{2\pi} Hz$
- D)  $\frac{10}{2\pi} Hz$

32. Power delivered by the source of the circuit becomes maximum, when:

- A)  $\omega L = \omega C$
- B)  $\omega L = \frac{1}{\omega C}$
- C)  $\omega L = -\left(\frac{1}{\omega C}\right)^2$
- D)  $\omega L = \sqrt{\omega C}$

33. An alternating voltage is connected in series with a resistance *R* and an inductance *L* . If the potential drop across the resistance is  $200V$  and across the inductance is  $150V$ , then the applied voltage is:

- A)  $350V$
- B)  $250V$
- C)  $500V$
- D)  $300V$





34. An inductive circuit contains resistance of  $10 \Omega$  and an inductance of  $20 H$ . If an  $AC$  voltage of  $120 V$  and frequency  $60 Hz$  is applied to this circuit, the current would be nearly:
- A)  $0.32 A$   
B)  $0.016 A$   
C)  $0.48 A$   
D)  $0.80 A$
35. Same current is flowing in two alternating circuits. The first circuit contains only inductance and the other contains only a capacitor. If the frequency of the *e. m. f.* of  $AC$  is increased, the effect on the value of the current will be:
- A) Increases in the first circuit and decreases in the other  
B) Increases in both the circuits  
C) Decreases in both the circuits  
D) Decreases in the first circuit and increases in the other
36. A capacitor is a perfect insulator for:
- A) Alternating currents  
B) Direct currents  
C) Both  $AC$  and  $DC$   
D) None of these
37. In a circuit containing an inductance of zero resistance, the *e. m. f.* of the applied  $AC$  voltage leads the current by:
- A)  $90^\circ$   
B)  $45^\circ$   
C)  $30^\circ$   
D)  $0.0^\circ$
38. In a pure inductive circuit or in an  $AC$  circuit containing inductance only, the current:
- A) *Leads the e. m. f. by  $90^\circ$*   
B) *Lags behind the e. m. f. by  $90^\circ$*   
C) *Sometimes leads and sometime lags behind the e. m. f.*  
D) *Is in phase with the e. m. f.*
39. A  $20 volts AC$  is applied to a circuit consisting of a resistance and a coil with negligible resistance. If the voltage across the resistance is  $12 V$ , the voltage across the coil is:
- A)  $16 V$   
B)  $10 V$   
C)  $8.0 V$   
D)  $6.0 V$





40. A resistance of  $300 \Omega$  and an inductance of  $1\pi H$  are connected in series to a  $AC$  voltage of  $20 V$  and  $200 Hz$  frequency. The phase angle between the voltage and current is:
- A)  $\tan^{-1}(\frac{4}{3})$   
 B)  $\tan^{-1}(\frac{3}{4})$   
 C)  $\tan^{-1}(\frac{3}{2})$   
 D)  $\tan^{-1}(\frac{2}{5})$
41. The power factor of  $LCR$  circuit at resonance is:
- A) 0.707  
 B) 1  
 C) Zero  
 D) 0.5
42. The natural frequency of a  $L - C$  circuit is equal to:
- A)  $\frac{1}{2\pi} \sqrt{LC}$   
 B)  $\frac{1}{2\pi\sqrt{LC}}$   
 C)  $\frac{1}{2\pi} \sqrt{\frac{L}{C}}$   
 D)  $\frac{1}{2\pi} \sqrt{\frac{C}{L}}$
43. An alternating voltage  $V = 200\sqrt{2} \sin(100t)$  is connected to a  $1\mu F$  capacitor through an  $AC$  ammeter. The reading of the ammeter shall be:
- A) 10 mA  
 B) 20 mA  
 C) 40 mA  
 D) 80 mA
44. An inductive circuit contains a resistance of  $10 \Omega$  and an inductance of  $2.0 H$ . If an  $AC$  voltage of  $120 V$  and frequency of  $60 Hz$  is applied to this circuit, the current in the circuit would be nearly:
- A) 0.32 A  
 B) 0.16 A  
 C) 0.48 A  
 D) 0.80 A
45. In a  $LCR$  circuit having  $L = 8.0 H$ ,  $C = 0.5 mF$  and  $R = 100 \Omega$  in series. The resonance frequency in radian/second is:
- A) 600  
 B) 400  
 C) 500  
 D) 300
46. In  $LCR$  circuit, the capacitance is changed from  $C$  to  $4C$ . For the same resonant frequency, the inductance should be changed from  $L$  to:
- A)  $2L$   
 B)  $L / 2$   
 C)  $L / 4$   
 D)  $4L$



47. A 120 volt AC source is connected across a pure inductor of inductance 0.70 H. If the frequency of the source is 60 Hz, the current passing through the inductor is:
- A) 4.55 A  
 B) 0.355 A  
 C) 0.455 A  
 D) 3.55 A
48. The impedance of a circuit consists of 3.0  $\Omega$  resistance and 4.0  $\Omega$  reactance. The power factor of the circuit is:
- A) 0.4  
 B) 0.6  
 C) 0.8  
 D) 1.0
49. L, C and R denote inductance, capacitance and resistance respectively. Pick out the combination which does not have the dimensions of frequency:
- A)  $\frac{1}{RC}$   
 B)  $\frac{R}{L}$   
 C)  $\frac{1}{\sqrt{LC}}$   
 D)  $\frac{C}{L}$
50. The power factor of a good choke coil is:
- A) Nearly zero  
 B) Exactly zero  
 C) Nearly one  
 D) Exactly one
51. If resistance of 100  $\Omega$  , inductance of 0.5 H and capacitance of  $10 \times 10^{-6} F$  are connected in series through 50 Hz AC supply, then impedance is:
- A) 1.876  $\Omega$   
 B) 18.76  $\Omega$   
 C) 189.7  $\Omega$   
 D) 101.3  $\Omega$
52. A 10  $\Omega$  resistance, 5 mH coil and 10 mF capacitor are joined in series. When a suitable frequency alternating current source is joined to this combination, the circuit resonates. If the resistance is halved, the resonance frequency:
- A) Is halved  
 B) Is doubled  
 C) Remains unchanged  
 D) In quadrupled



53. In a series circuit  $R = 300 \Omega$ ,  $L = 0.9 H$ ,  $C = 2.0 mF$  and  $\omega = 1000 \text{ rad/sec}$ . The impedance of the circuit is:
- A)  $1300 \Omega$   
 B)  $900 \Omega$   
 C)  $500 \Omega$   
 D)  $400 \Omega$
54. In a  $L - R$  circuit, the value of  $L$  is  $(\frac{0.4}{\pi}) H$  and the value of  $R$  is  $30 \Omega$ . If in the circuit, an alternating *e. m. f.* of  $200 V$  at  $50 \text{ cycles per sec}$  is connected, the impedance of the circuit and current will be:
- A)  $11.4 \Omega$ ,  $17.5 A$   
 B)  $30.7 \Omega$ ,  $6.5 A$   
 C)  $40.4 \Omega$ ,  $5.0 A$   
 D)  $50 \Omega$ ,  $4.0 A$
55. The reactance of a coil when used in the domestic AC power supply ( $220 \text{ volt}$ ,  $50 \text{ Hz}$ ) is  $100 \Omega$ . The self inductance of the coil is nearly:
- A)  $3.2 H$   
 B)  $0.32 H$   
 C)  $2.2 H$   
 D)  $0.22 H$
56. The reactance of a  $25 \mu F$  capacitor at the ac frequency of  $4000 \text{ Hz}$  is:
- A)  $\frac{5}{\pi} \Omega$   
 B)  $\sqrt{\frac{5}{\pi}} \Omega$   
 C)  $10.0 \Omega$   
 D)  $\sqrt{10.0} \Omega$
57. The frequency for which a  $5 \mu F$  capacitor has a reactance of  $\frac{1}{1000} \Omega$  is given by:
- A)  $\frac{100}{\pi} \text{ MHz}$   
 B)  $\frac{1000}{\pi} \text{ Hz}$   
 C)  $\frac{1}{1000} \text{ Hz}$   
 D)  $1000 \text{ Hz}$
58. An *e. m. f.*  $V = 4.0 \cos(1000t) \text{ volt}$  is applied to an  $LR - \text{circuit}$  of inductance  $3 \text{ mH}$  and resistance  $4 \Omega$ . The amplitude of current in the circuit is:
- A)  $\frac{4}{\sqrt{7}} A$   
 B)  $1.0 A$   
 C)  $\frac{4}{7} A$   
 D)  $0.8 A$



59. In an ac circuit, a resistance of  $R$  ohm is connected in series with an inductance  $L$ . If phase angle between voltage and current be  $45^\circ$ , the value of inductive reactance will be:
- $\frac{R}{4}$
  - $\frac{R}{2} Hz$
  - $R$
  - Cannot be found with the given data
60. The phase difference between the current and voltage of LCR circuit in series combination at resonance is:
- 0
  - $\pi/2$
  - $\pi$
  - $-\pi$
61. In a series resonant circuit, the AC voltage across resistance  $R$ , inductance  $L$  and capacitance  $C$  are  $5 V$ ,  $10 V$  and  $10 V$  respectively. The AC voltage applied to the circuit will be:
- 20 V
  - 10 V
  - 5 V
  - 25 V
62. When 100 volt DC is applied across a coil, a current of 1.0 A flows through it. When 100 volt AC at 50 Hz is applied to the same coil, only 0.5 A current flows. The impedance of the coil is:
- 100Ω
  - 200Ω
  - 300Ω
  - 400Ω
63. For series LCR circuit, wrong statement is:
- Applied *e. m. f.* and potential difference across resistance are in same phase
  - Applied *e. m. f.* and potential difference at inductor coil have phase difference of  $\pi/2$
  - Potential difference at capacitor and inductor have phase difference of  $\pi/2$
  - Potential difference across resistance and capacitor have phase difference of  $\pi/2$
64. In a purely resistive ac circuit, the current:
- Lags behind the *e. m. f.* in phase
  - Is in phase with the *e. m. f.*
  - Leads the *e. m. f.* in phase
  - Leads the *e. m. f.* in half the cycle and lags behind it in the other half
65. A  $12 \Omega$  resistor and a  $0.21 H$  inductor are connected in series to an ac source operating at 20 V, 50 cycle/second. The phase angle between the current and the source voltage is:
- $30^\circ$
  - $40^\circ$
  - $80^\circ$
  - $90^\circ$





66. The resonant frequency of a circuit is  $f$ . If the capacitance is made 4 times the initial values, then the resonant frequency will become:
- A)  $f / 2$
  - B)  $2f$
  - C)  $f$
  - D)  $f / 4$
67. In the non-resonant circuit, what will be the nature of the circuit for frequencies higher than the resonant frequency:
- A) Resistive
  - B) Capacitive
  - C) Inductive
  - D) None of the above
68. In an AC circuit, the potential difference across an inductance and resistance joined in series are respectively 16 V and 20 V. The total potential difference across the circuit is:
- A) 20.0 V
  - B) 25.6 V
  - C) 31.9 V
  - D) 53.5 V
69. An LCR circuit contains  $R = 50 \Omega$ ,  $L = 1 \text{ mH}$  and  $C = 0.1 \text{ mF}$ . The impedance of the circuit will be minimum for a frequency of:
- A)  $\frac{10^5}{2\pi} \text{ s}^{-1}$
  - B)  $\frac{10^6}{2\pi} \text{ s}^{-1}$
  - C)  $2\pi \times 10^5 \text{ s}^{-1}$
  - D)  $2\pi \times 10^6 \text{ s}^{-1}$
70. In a series LCR circuit, resistance  $R = 10\Omega$  and the impedance  $Z = 20\Omega$ . The phase difference between the current and the voltage is:
- A)  $30^\circ$
  - B)  $45^\circ$
  - C)  $60^\circ$
  - D)  $90^\circ$
71. A series ac circuit consist of an inductor and a capacitor. The inductance and capacitance are respectively 1 H and  $25\mu\text{F}$ . If the current is maximum in circuit, then angular frequency will be:
- A) 200
  - B) 100
  - C) 50
  - D)  $200/2\pi$




72. An alternating *e. m. f.* of frequency ( $f = \frac{1}{2\pi\sqrt{LC}}$ ) is applied to a series LCR circuit. For this frequency of the applied *e. m. f.*:

- A) The circuit is at resonance and its impedance is made up only of a reactive part
- B) The current in the circuit is in phase with the applied *e. m. f.* and the voltage across R equals this applied *emf*
- C) The sum of the potential difference across the inductance and capacitance equals the applied *e. m. f.* which is  $180^\circ$  ahead of phase of the current in the circuit
- D) The quality factor of the circuit is  $(\frac{\omega L}{R})$  or  $(\frac{1}{\omega CR})$  and this is a measure of the voltage magnification (produced by the circuit at resonance) as well as the sharpness of resonance of the circuit

73. In the circuit shown below, the AC source has voltage  $V = 20\cos(\omega t)$  volts with  $\omega = 2000$  rad/sec. the amplitude of the current will be nearest to:

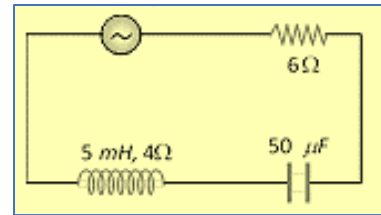- A) 2.0 A
- B) 3.3 A
- C)  $\frac{2}{\sqrt{5}}$
- D)  $\sqrt{5}$  A



74. The quality factor of LCR circuit having resistance (R) and inductance (L) at resonance frequency ( $\omega$ ) is given by:

- A)  $\frac{\omega L}{R}$
- B)  $\frac{R}{\omega L}$
- C)  $(\frac{\omega L}{R})^{1/2}$
- D)  $(\frac{\omega L}{R})^2$

75. Power factor is maximum in an LCR circuit when:

- A)  $X_L = X_C$
- B)  $R = 0$
- C)  $X_L = 0$
- D)  $X_C = 0$

76. In an AC circuit the reactance of a coil is  $\sqrt{3}$  times its resistance, the phase difference between the voltage across the coil to the current through the coil will be:

- A)  $\pi/3$
- B)  $\pi/2$
- C)  $\pi/4$
- D)  $\pi/6$



77. The capacity of a pure capacitor is 1 farad. In dc circuits, its effective resistance will be:
- A) Zero
  - B) Infinite
  - C)  $1.0 \Omega$
  - D)  $0.5 \Omega$
78. In an AC circuit, the current lags behind the voltage by  $\pi/3$ . The components in the circuit are:
- A) R and L
  - B) R and C
  - C) L and C
  - D) Only R
79. In an AC circuit, the power factor:
- A) Is zero when the circuit contains an ideal resistance only
  - B) Is unity when the circuit contains an ideal resistance only
  - C) Is zero when the circuit contains an ideal inductance only
  - D) Is unity when the circuit contains an ideal inductance only
80. For high frequency, a capacitor offers:
- A) More reactance
  - B) Less reactance
  - C) Zero reactance
  - D) Infinite reactance
81. The coil in a circuit:
- A) Increases the current
  - B) Decreases the current
  - C) Does not change the current
  - D) Has high resistance to dc circuit
82. In a circuit, the current lags behind the voltage by a phase difference of  $\pi/2$ . The circuit contains which of the following:
- A) Only R
  - B) Only L
  - C) Only C
  - D) R and C





83. The inductive reactance of an inductor of  $1\pi$  henry at 50 Hz frequency is:
- A)  $\frac{50}{\pi}\Omega$
  - B)  $\frac{\pi}{50}\Omega$
  - C)  $100\Omega$
  - D)  $50\Omega$
84. An oscillator circuit consists of an inductance of  $0.5mH$  and a capacitor of  $20\mu F$ . The resonant frequency of the circuit is nearly:
- A)  $15.92 Hz$
  - B)  $159.2 Hz$
  - C)  $1592 Hz$
  - E)  $15910 Hz$
85. Reactance of a capacitor of capacitance  $C\mu F$  for AC frequency  $\frac{400}{\pi} Hz$  is  $25\Omega$ . The value C is:
- A)  $50\mu F$
  - B)  $25\mu F$
  - C)  $100\mu F$
  - D)  $75\mu F$
86. There is a  $5.0\Omega$  resistance in an AC, circuit. Inductance of  $0.1H$  is connected with it in series. If equation of ac *e. m. f.* is  $5.0\sin 50t$  then the phase difference between current and *e. m. f.* is:
- A)  $\frac{\pi}{2}$
  - B)  $\frac{\pi}{6}$
  - C)  $\frac{\pi}{4}$
  - D)  $0.0$
87. In a AC circuit of capacitance the current from potential is:
- A) Forward
  - B) Backward
  - C) Both are in the same phase
  - D) None of these





88. In an LCR circuit capacitance is changed from  $C$  to  $2C$ . For the resonant frequency to remain unchanged, the inductance should be change from  $L$  to:


- A)  $4L$
- B)  $2L$
- C)  $L/2$
- D)  $L/4$

89. The current in series LCR circuit will be maximum when  $\omega$  is:

- A) As large as possible
- B) Equal of natural frequency of LCR system
- C)  $\sqrt{LC}$
- D)  $\sqrt{1/LC}$


90. An inductor  $L$  and a capacitor  $C$  are connected in the circuit as shown in the figure. The frequency of the power supply is equal to the resonant frequency of the circuit. Which ammeter will read zero ampere?

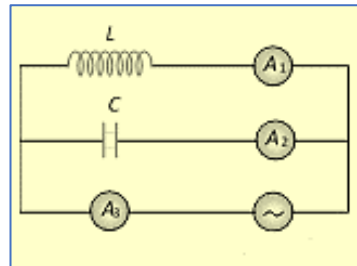- A)  $A_1$
- B)  $A_2$
- C)  $A_3$
- D) None of these



91. For the series LCR circuit shown in the figure, what is the resonance frequency and the amplitude of the current at the resonating frequency:

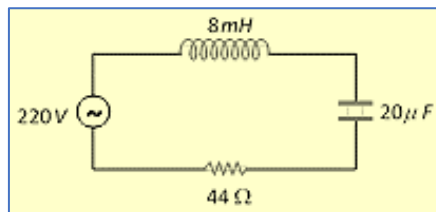- A)  $2500 \text{ rad s}^{-1}$  and  $5\sqrt{2} \text{ A}$
- B)  $2500 \text{ rad s}^{-1}$  and  $5 \text{ A}$
- C)  $2500 \text{ rad s}^{-1}$  and  $\frac{5}{\sqrt{2}} \text{ A}$
- D)  $25 \text{ rad s}^{-1}$  and  $5\sqrt{2} \text{ A}$




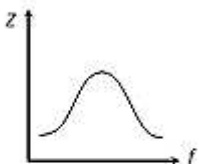
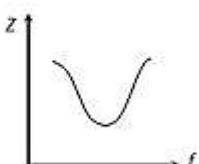
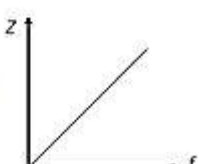
92. In an A.C. circuit the current:

- A) Always leads the voltage
- B) Always lags behind the voltage
- C) Is always in phase with the voltage
- D) May lead or lag behind or be in phase with the voltage

93. Which of the following components of a LCR circuit, with ac supply, dissipates energy:


- A) L
- B) R
- C) C
- D) All of these

94. Which one of the following curves represents the variation of impedance ( $Z$ ) with frequency  $f$  in series LCR circuit?

- A) 
- B) 
- C) 
- D) 


95. The variation of the instantaneous current ( $i$ ) and the instantaneous  $emf$  in a circuit is as shown in fig. Which of the following statements is correct?

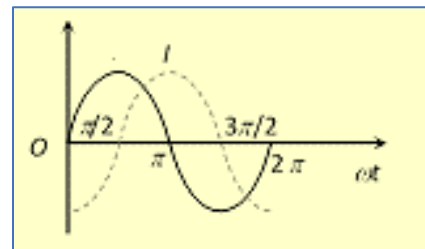- A) The voltage lags behind the current by  $\pi / 2$
- B) The voltage leads the current by  $\pi / 2$
- C) The voltage and the current are in phase
- D) The voltage leads the current by  $\pi$




96. The figure shows variation of  $R$ ,  $X_L$  and  $X_C$  with frequency  $f$  in a series L, C, R circuit. Then for what frequency point, the circuit is inductive:


- A) A
- B) B
- C) C
- D) All points

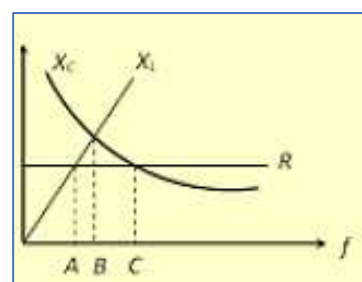

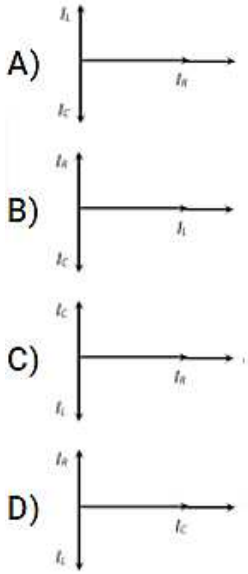97. An alternating  $emf$  is applied across a parallel combination of a resistance  $R$ , capacitance  $C$  and an inductance  $L$ . If  $i_R, i_L, i_C$  are the currents through  $R, L$  and  $C$  respectively, then the diagram which correctly represents, the phase relationship among  $i_R, i_L, i_C$  and source  $emf$ , is given by:




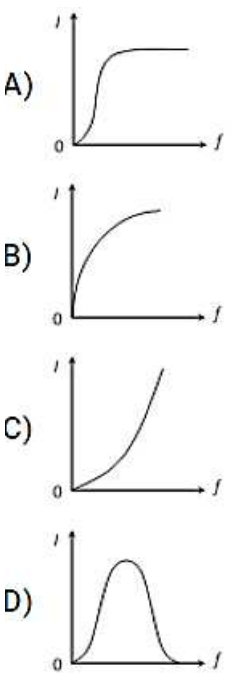98. An ac source of variable frequency  $f$  is connected to an  $LCR$  series circuit. Which one of the graphs in figure. represents the variation of current of current  $i$  in the circuit with frequency  $f$ :




99. The *r. m. s.* voltage of the wave form shown is:

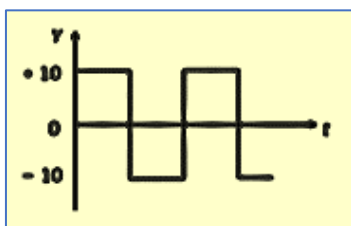- A) 10 V
- B) 7 V
- C) 6.37 V
- D) None of these




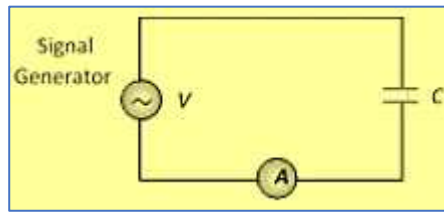100. A constant voltage at different frequencies is applied across a capacitance  $C$  as shown in the figure. Which of the following graphs Correctly depicts the variation of current with frequency?




- A)
- B)
- C)
- D)

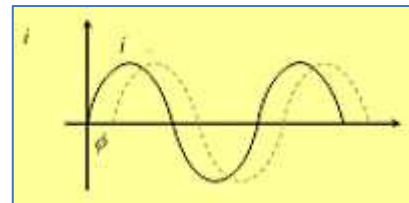101. When an AC source of *e. m. f.*  $V = V_0 \sin(100t)$  is connected across a circuit, the phase difference between the *e. m. f.*  $V$  and the current  $i$  in the circuit is observed to be  $\pi/4$ , as shown in the diagram. If the circuit consists possibly only of RC or LC in series, find the relationship between the two elements:




- A)  $R = 1.0k \Omega, C = 10.0\mu F$
- B)  $R = 1.0k \Omega, C = 1.0\mu F$
- C)  $R = 1.0k \Omega, L = 10.0H$
- D)  $R = 1.0k \Omega, L = 1.0H$

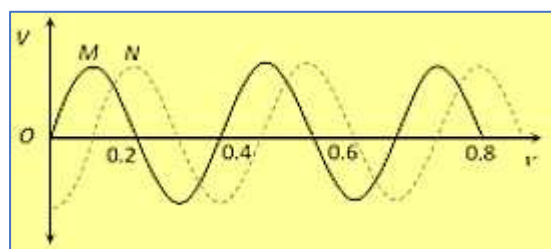102. Two sinusoidal voltages of the same frequency are shown in the diagram. What is the frequency in Hz, and the phase relationship? If Frequency Phase M lead of N.



- A) 0.4,  $-\pi/4$
- B) 2.5,  $-\pi/2$
- C) 2.5,  $+\pi/2$
- D) 2.5,  $-\pi/4$

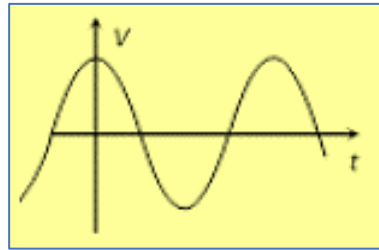103. The voltage across a pure inductor is represented by the following diagram. Which one of the following diagrams will represent the current?



- A)
- B)
- C)
- D)


104. In pure inductive circuit, the curves between frequency  $f$  and reciprocal of inductive reactance  $(\frac{1}{X_L})$  is:

- A)
- B)
- C)
- D)




105. The vector diagram of current and voltage for a circuit is as shown. The components of the circuit will be

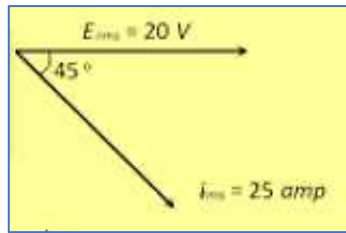- A) LCR
- B) LR
- C) LCR or LR
- D) None of these



106. The resonance point in  $(XL - f)$  and  $(XC - f)$  curves is

- A) P
- B) Q
- C) R
- D) S

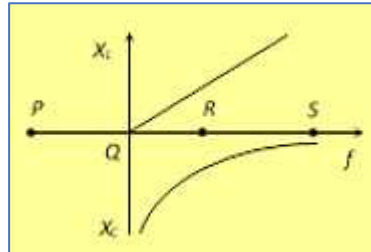


107. The  $(i - f)$  curve for anti-resonant circuit is:

- A)
- B)
- C)
- D)


108. The graphs given below depict the dependence of two reactive impedances  $X_1$  and  $X_2$  on the frequency of the alternating *e. m. f.* applied individually to them. We can then say that:

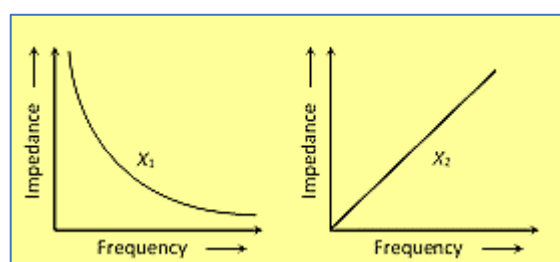- A)  $X_1$  is an inductor and  $X_2$  is a capacitor
- B)  $X_1$  is a resistor and  $X_2$  is a capacitor
- C)  $X_1$  is a capacitor and  $X_2$  is an inductor
- D)  $X_1$  is an inductor and  $X_2$  is a resistor



109. Which of the following plots may represent the reactance of a series LC combination:

- A) a
- B) b
- C) c
- D) d

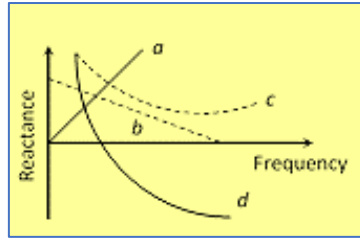


110. Which of the following curves correctly represents the variation of capacitive reactance  $X_C$  with frequency  $f$ :

- A)
- B)
- C)
- D)


111. In the circuit given below, what will be the reading of the voltmeter:

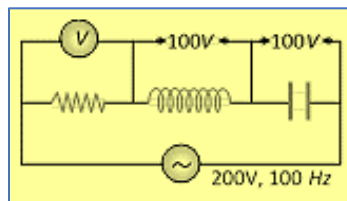- A) 300 V
- B) 900 V
- C) 200 V
- D) 400 V



112. In the circuit shown below, what will be the readings of the voltmeter and ammeter:

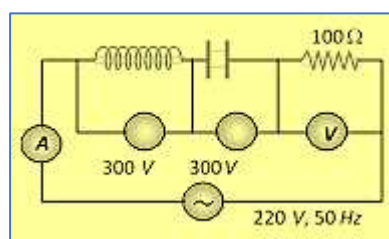- A) 800 V, 2A
- B) 300 V, 2A
- C) 220 V, 2.2 A
- D) 100 V, 2A



113. A bulb and a capacitor are connected in series to a source of alternating current. If its frequency is increased, while keeping the voltage of the source constant, then:

- A) Bulb will give more intense light
- B) Bulb will give less intense light
- C) Bulb will give light of same intensity as before
- D) Bulb will stop radiating light

114. The voltage of an AC source varies with time according to the equation  $V = 100\sin 100\pi t \cos 100\pi t$  where t is in seconds and V is in volts. Then:


- A) The peak voltage of the source is 100 V
- B) The peak voltage of the source is 50 V
- C) The peak voltage of the source is  $\frac{100}{\sqrt{2}}$  V
- D) The frequency of the source is 50 Hz

115. The diagram shows a capacitor C and a resistor R connected in series to an AC source.  $V_1$  and  $V_2$  are voltmeters and A is an ammeter. Consider now the following statements

- I. Readings in A and  $V_2$  are always in phase
- II. Reading in  $V_1$  is ahead in phase with reading in  $V_2$
- III. Readings in A and  $V_1$  are always in phase


which of these statements are/is correct?

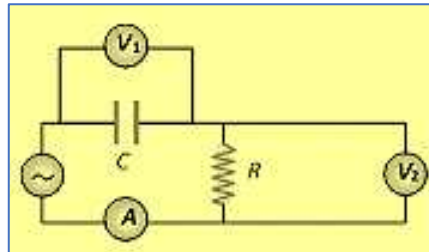- A) I only
- B) II only
- C) I and II only
- D) II and III only




116. In the circuit shown in figure neglecting source resistance the voltmeter and ammeter reading will respectively, will be:

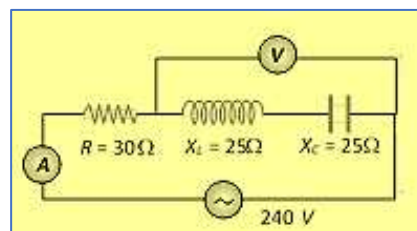- A) 0V, 3A
- B) 150V, 3A
- C) 150V, 6A
- D) 0V, 8A





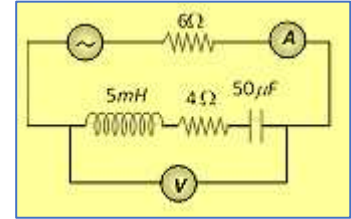
117. In the circuit shown in the figure, the AC source gives a voltage  $V = 20\cos(2000t)$ . Neglecting source resistance, the voltmeter and ammeter reading will be:



- A) 0V, 0.47A
- B) 1.68V, 0.47A
- C) 0V, 1.4 A
- D) 5.6V, 1.4 A

118. In the adjoining AC circuit the voltmeter whose reading will be zero at resonance is:

- A) V1
- B) V2
- C) V3
- D) V4

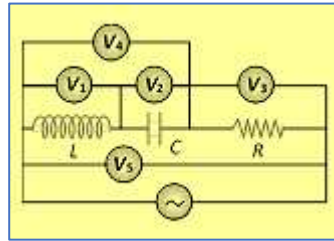


119. For a series RLC circuit  $R = X_L = 2X_C$ . The impedance of the circuit and phase difference (between) V and i will be:

- A)  $\frac{\sqrt{5} R}{2}, \tan^{-1}(2)$
- B)  $\frac{\sqrt{5} R}{2}, \tan^{-1}(\frac{1}{2})$
- C)  $\sqrt{5} X_C, \tan^{-1}(2)$
- D)  $\sqrt{5} R, \tan^{-1}(\frac{1}{2})$

120. In the adjoining figure the impedance of the circuit will be

- A) 120 Ω
- B) 50 Ω
- C) 60 Ω
- D) 90 Ω

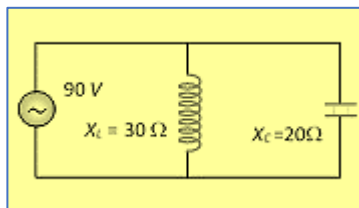

121. The reading of ammeter in the circuit shown will be

- A) 2A
- B) 2.4 A
- C) Zero
- D) 1.7 A

