

تم تحميل هذا الملف من موقع المناهج الإماراتية



*للحصول على أوراق عمل لجميع الصفوف وجميع المواد اضغط هنا

<https://almanahj.com/ae>

* للحصول على أوراق عمل لجميع مواد الصف الحادي عشر اضغط هنا <https://almanahj.com/ae/11design>

* للحصول على جميع أوراق الصف الحادي عشر في مادة تصميم ولجميع الفصول, اضغط هنا

<https://almanahj.com/ae/11design>

* للحصول على أوراق عمل لجميع مواد الصف الحادي عشر في مادة تصميم الخاصة بـ الفصل الثاني اضغط هنا

<https://almanahj.com/ae/11design2>

* لتحميل كتب جميع المواد في جميع الفصول للـ الصف الحادي عشر اضغط هنا [grade11/ae/com.almanahj//:https](https://almanahj.com/ae/grade11)

للتحدث إلى بوت المناهج على تلغرام: اضغط هنا [bot_almanahj/me.t//:https](https://t.me/bot_almanahj)



STUDENT SECTION

Name				Class	
Student MOE number (SIS)		School MOE Number		STUDENT SIGNATURE	
School name					

PLEASE NOTE – This SAMPLE paper is to guide students on question types ONLY. It may not reflect the content for the final examination. Please refer to the coverage documents.
Section 3 - Q2 – Requires colour printing QR for the Resistor colour coding chart to be displayed.

Creative Design & Innovation

11 General

Sample - Term 2

Date: February 2018

Time: TBC

Duration: 35 minutes

STUDENT INSTRUCTIONS –

Students must attempt **all** questions.
For this examination, you must have:

1. An ink pen – blue.
2. A pencil.
3. A ruler.

TEACHER NOTES & INSTRUCTIONS

Please tick ✓ the correct answers in **RED INK** and then write the mark awarded in the marking columns. With multiple mark answers highlight where the mark is awarded by **underlining** or by using an extra tick.

FOR ADMIN ONLY

MARKING RECORD

Section	Section TOTALS
Section 1	
Section 2	
Section 3	
MARKER SIGNATURE	TOTAL MARKS
MODERATOR SIGNATURE	

SECTION 1 – Multiple choice

Choose and circle the correct answer – A, B, C or D.

(1 mark each)

Example: An electrical component which opens or closes a circuit.

- A. speaker
- B. bulb
- C. switch
- D. battery

1. Electrical circuits require the flow of _____.
 - A. newtons
 - B. electrons
 - C. protons
 - D. neutrons
2. What is an LED?
 - A. Light Even Diode
 - B. Light Engaged Diode
 - C. Light Emerging Diode
 - D. Light Emitting Diode
3. Analogue signals have _____ values.
 - A. infinite
 - B. limited
 - C. defined
 - D. additional
4. Digital signals use _____.
 - A. 1's & 2's
 - B. -1 & 0
 - C. -1 & +1
 - D. 0's & 1's
5. Which letter represents current in Ohm's Law?
 - A. C
 - B. V
 - C. I
 - D. O

SECTION 2 – True or False

Choose and circle the correct answer TRUE or FALSE.

(1 mark each)

Example:

- An input is information or data entered in a system

TRUE

FALSE

1. Continuity mode on a Multimeter uses a diode symbol

TRUE

FALSE

2. A Multimeter can measure Watts

TRUE

FALSE

3. A microcontroller is a single chip microcomputer

TRUE

FALSE

4. A microcontroller only uses RAM memory

TRUE

FALSE

5. Processing is a series of actions leading to a result

TRUE

FALSE

/ 5

SECTION 3 – Core content

1 – Complete the sentences below using **ONE** word for each.


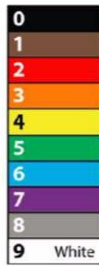
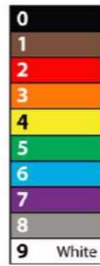

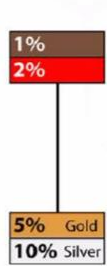
Do not use the same word for more than one answer. **TWO** words will **NOT** be used.

coil	load	current	solid	switch	driver	sensing
------	------	---------	-------	--------	--------	---------





- a. A relay is an electromagnetic _____.
- b. Every relay has a _____ unit.
- c. In a relay there is a control circuit and a _____ circuit.
- d. The control circuit controls the _____ in the other circuit.
- e. A _____ state relay is made from semiconductor materials.

/ 5

2a – Identify columns A & B shown in the resistor colour code table below. (2 marks)


1 st Digit	2 nd Digit	3 rd Digit	A	B
				
Colour Code Table				
			A	
			B	

2b – What are the values of the resistors shown below. (4 marks)

 <p>Red / green / yellow / gold</p>	A	
 <p>White / violet / yellow / gold</p>	B	
 <p>Green / blue / red / gold</p>	C	
 <p>Green / violet / red / black / red</p>	D	

2c – In the box below write the formulae used to calculate Ohm's Law. (2 marks)

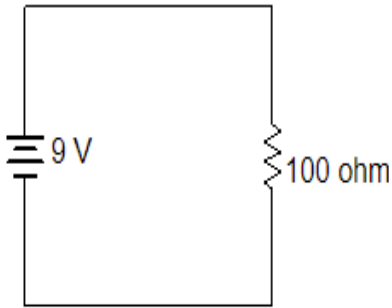2d – Calculate the current flowing through the resistor in this circuit using Ohm’s Law.





(2 marks)

/ 10

3 – Match the words with their definition or image.

(5 marks)

Write the matching letter in the correct box. The first one has been done for you.

TERM / COMPONENT	Symbol letter	SYMBOL / COMPONENT	
1. Battery	F		A
2. Digital signal		Ω	B
3. Analog signal		Central computer chip which acts as a brain in a system.	C
4. Bulb			D
5. CPU		A source of light energy	E
6. Ohms		An electrical DC power source.	F

/ 5

You have now finished the examination.

TOTAL
/ 30